

# Lab 10

## Hazard Unit Design

# What is hazard unit?

- No structural hazard.
- Only data and control hazards.
- FSM (Finite State Machine) that generates 3 signals (PCWrite, IFWriet, Bubble)

# Data Hazards

- Need to keep destination register of past 3 instruction.
- Compare with current register  $R_A$  and  $R_B$ .
- Never have a hazard from \$0.
- If  $R_A$  or  $R_B$  are not being used set them to 0.
- Immediate type of instruction  $R_B$  is valid?

# Data Hazards (Bubble)

- Bubble should be 1 if current instruction is reading one of the registers that was destination by previous any of the previous three instructions.
- Hold Bubble high for appropriate amount of time.
- If `cmp1=1` then generate 3 cycles of bubble.
- If `cmp2=1` then generate 2 cycles of bubble.
- If `cmp3=1` then generate 1 cycle of bubble.
- If Bubble is one the current instruction is not to be executed until Bubble is set to 0. (`PCWrite=IFWrite=0`)


```
cmp1 = (((rs==rw1) || (rt==rw1)) && (rw1 != 0)) ? 1:0
cmp2 = (((rs==rw2) || (rt==rw2)) && (rw2 != 0)) ? 1:0
cmp3 = (((rs==rw3) || (rt==rw3)) && (rw3 != 0)) ? 1:0
```

# Control Hazards


- Use PCWrite and IFWrite to handle the hazard.
- If Jump=1 then PCWrite=0 for 1 cycles.
- If Branch=1 then PCWrite=0 for 2 cycles.
- IFWrite must be 0 for one additional cycle than PCWrite unless the instruction is a branch, and branch is **Not taken**.
- Pay attention to signal priorities.

**{Jump,Branch,ALUZero4,Comp1,Comp2,Comp3}/{PCWrite,IFWrite,Bubble}**


**Normal:  
6'b00x000/3'b110**

 

 **{Jump,Branch,ALUZero4,Comp1,Comp2,Comp3}/{PCWrite,IFWrite,Bubble}**




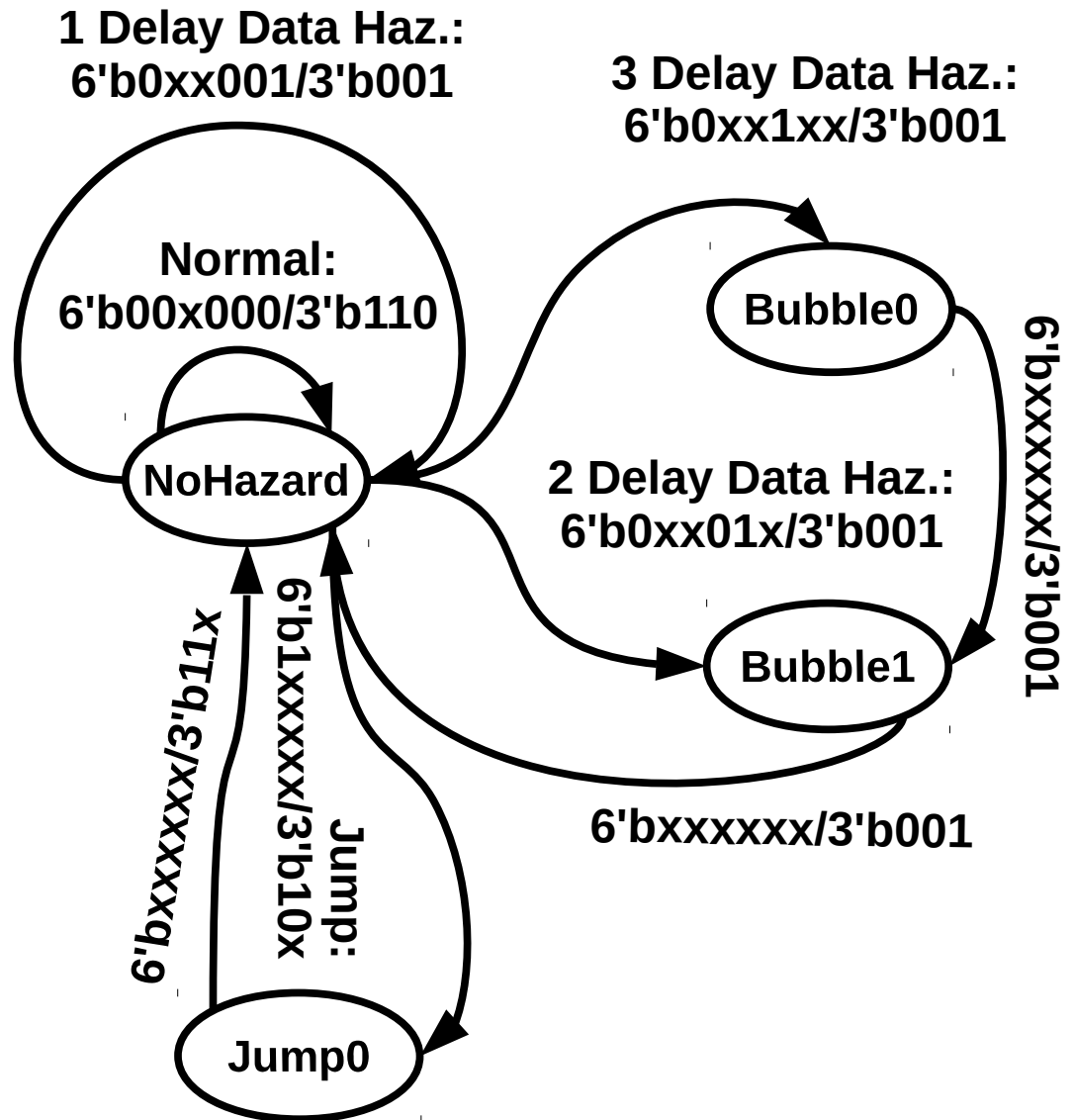{Jump,Branch,ALUZero4,Comp1,Comp2,Comp3}/{PCWrite,IFWrite,Bubble}





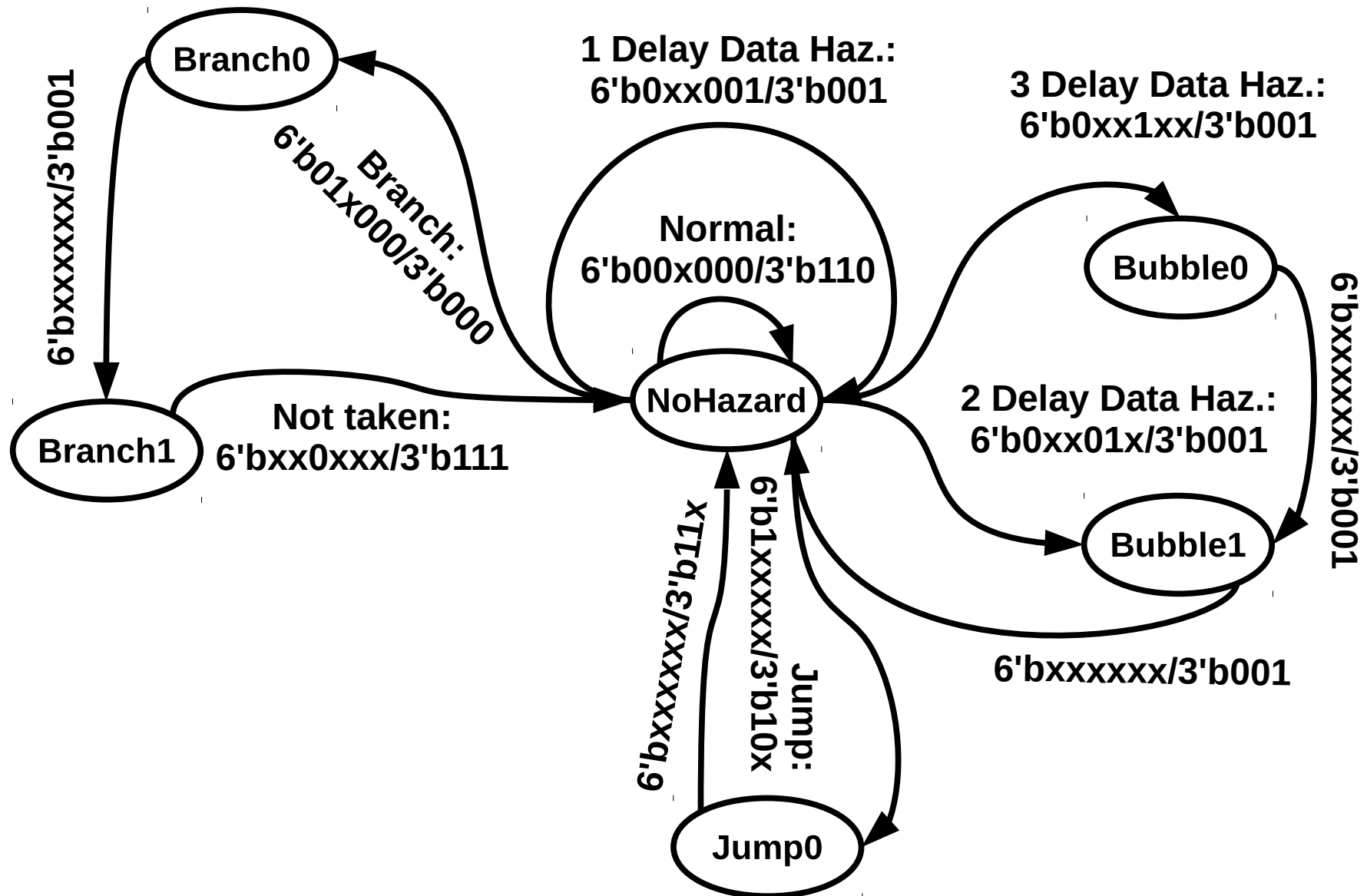{Jump,Branch,ALUZero4,Comp1,Comp2,Comp3}/{PCWrite,IFWrite,Bubble}



{Jump,Branch,ALUZero4,Comp1,Comp2,Comp3}/{PCWrite,IFWrite,Bubble}

